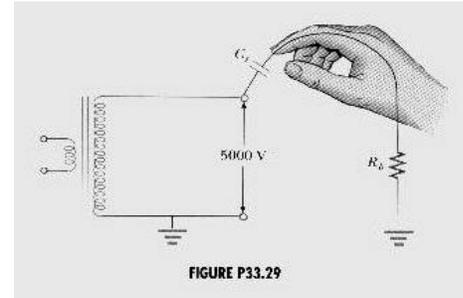


- [based on Serway Chapter 33 Question 4, pg 984]
  - Explain how the acronym “ELI the ICE man” can be used to recall whether current leads voltage or voltage leads current in RLC circuits.
  - Why does the lead / lag exist for capacitors and inductors? Explain using physical reasoning / analogies.
  - What causes the lead / lag mathematically?




- [Serway Chapter 33 Problem 29, pg 987]
 

A person is working near the secondary of a transformer, as shown in the figure. The primary voltage is 120 V at 60.0 Hz. The capacitance  $C_s$ , which is the capacitance between hand and secondary winding, is 20.0 pF. Assuming the person has a body resistance to ground  $R_b = 50.0 \text{ k}\Omega$ , determine the rms voltage across the body. (Hint: Redraw the circuit with the secondary of the transformer as a simple ac source.)

- [Serway Chapter 33 Problem 30, pg 988]
 

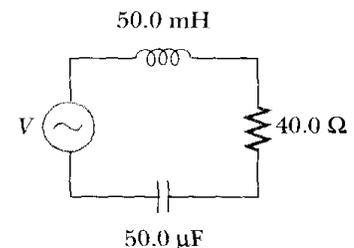The voltage source in the figure has an output  $V_{\text{rms}} = (100\text{V}) \cos(1000t)$ . Determine (a) the current in the circuit and (b) the power supplied by the source. (c) Show that the power dissipated in the resistor is equal to the power supplied by the source.



- [Serway Chapter 33 Problem 48, pg 989]
 

A series RLC circuit has the following values:  $L = 20.0 \text{ mH}$ ,  $C = 100 \text{ }\mu\text{F}$ ,  $R = 20.0 \text{ }\Omega$  and  $V_{\text{max}} = 100 \text{ V}$ , with  $v = V_{\text{max}} \sin \omega t$ . Find (a) the resonance frequency, (b) the amplitude of the current at the resonance frequency, (c) the Q of the circuit, and (d) the amplitude of the voltage across the inductor at resonance.
- [based on Serway Chapter 33 Problem 61, pg 990]
 

A step-down transformer is used for running / recharging the batteries of portable devices such as tape players. The turns ratio inside the transformer is 13:1 and is used with 120-V (rms) household service. If a particular tape player draws 0.35 A from the household outlet, what are (a) the voltage and (b) the current supplied from the transformer? (c) How much power is delivered?
- [Serway Chapter 33 Problem 71, pg 990]
 

A transmission line that has a resistance per unit length of  $4.50 \times 10^{-4} \text{ }\Omega / \text{m}$  is to be used to transmit 5.00 MW over 400 miles ( $6.44 \times 10^5 \text{ m}$ ). The output voltage of the generator is 4.5 kV. (a) What is the line loss if a transformer is used to step up the voltage to 500 kV? (b) What fraction of the input power is lost to the line under these circumstances? (c) What difficulties would be encountered on attempting to transmit 5.00 MW at the generator voltage of 4.5 kV?