

Name: _____

ID: _____

ENGINEERING 2C03

DAY CLASS

Dr. Wm. Garland

DURATION: 50 minutes

McMASTER UNIVERSITY MIDTERM EXAMINATION

February 27, 2001

Special Instructions:

1. Closed Book. All calculators and up to 6 single sided 8 1/2" by 11" crib sheets are permitted.
2. Do all questions. Place your answers on the exam sheets; use additional pages if necessary.
3. The value of each part is as indicated. TOTAL Value: 100 marks

THIS EXAMINATION PAPER INCLUDES 3 PAGES AND 3 QUESTIONS. YOU ARE RESPONSIBLE FOR ENSURING THAT YOUR COPY OF THE PAPER IS COMPLETE. BRING ANY DISCREPANCY TO THE ATTENTION OF YOUR INVIGILATOR.

1. [30 marks total] Suppose that the current through a conductor decreases exponentially with time according to


$$I(t) = I_0 e^{-t/\tau}$$

where I_0 is the initial current (at $t=0$), and τ is the time constant having dimensions of time. Consider a fixed observation point within the conductor. How much charge passes this point between $t=0$ and $t=\tau$?

Sol'n:

$$\begin{aligned} I &= \frac{dQ}{dt} \Rightarrow Q = \int_0^{\tau} I dt = I_0 \int_0^{\tau} e^{-t/\tau} dt \\ &= -\tau e^{-t/\tau} \Big|_0^{\tau} = \tau (1 - e^{-1}) \\ &= 0.6321 I_0 \tau \end{aligned}$$

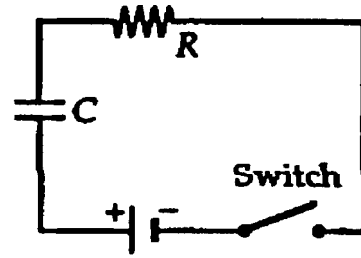2. [30 marks] Consider a series RC circuit, as shown in the figure, for which $R = 1.00 \text{ M}\Omega$, $C = 5.00 \text{ }\mu\text{F}$, and $\varepsilon = 30.0 \text{ V}$.
- Find the time constant of the circuit.
 - Find the maximum charge on the capacitor after the switch is closed.
 - If the switch is closed at $t = 0$, find the current in the resistor 10.0 s later.



Sol'n:

We have $\varepsilon - q/c - IR = 0$, $I = \frac{dq}{dt}$

$$\Rightarrow \frac{dq}{dt} = \varepsilon/R - q/Rc \Rightarrow q = \varepsilon C (1 - e^{-t/\tau})$$



$$I = \varepsilon/R e^{-t/Rc} \quad ; \quad \tau = RC$$

$$\therefore \text{a) } \tau = RC = 1 \times 10^6 \times 5 \times 10^{-6} = \underline{5.00 \text{ s}}$$

$$\text{b) at } t = \infty, \quad q = \varepsilon C = 5 \times 10^{-6} \times 30 = \underline{150 \text{ }\mu\text{C}}$$

$$\text{c) } I = \frac{30}{1 \times 10^6} e^{-10/5} = 4.06 \times 10^{-6} \text{ A} = \underline{4.06 \text{ }\mu\text{A}}$$

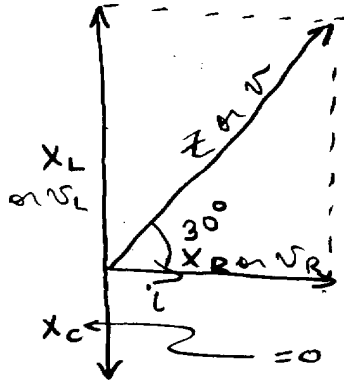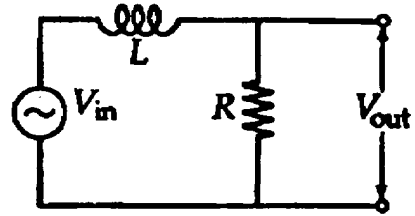3. [40 marks] Consider the phase-shifter circuit shown in the figure. The input voltage is described by the expression $v = (10 \text{ V}) \sin 200t$ (in SI units). Assuming that $L = 500 \text{ mH}$.
- Find the value of R such that the output voltage v_{out} lags behind the input voltage by 30° .
 - Find the amplitude of the output voltage.



$$a) \tan 30^\circ = \frac{X_L - X_C}{X_R} = \frac{X_L}{X_R}$$

$$\therefore R = \frac{X_L}{\tan 30^\circ} = \frac{\omega L}{\tan 30^\circ} = \frac{200 \text{ rad/s} \times 0.5 \text{ H}}{\tan 30^\circ}$$

$$= 173 \Omega$$

$$b) \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{iR}{iZ} = \frac{R}{\sqrt{R^2 + X_L^2}}$$

$$\therefore V_{\text{out}} = \frac{10 \times 173}{\sqrt{173^2 + 100^2}} = 8.66 \text{ V}$$