

## ENGINEERING 203

DAY CLASS

Dr. Wm. Garland

DURATION: 50 minutes

McMASTER UNIVERSITY MIDTERM EXAMINATION

February 24, 1999

---

### Special Instructions:

1. Closed Book. All calculators and up to 3 single sided 8 ½" by 11" crib sheets are permitted.
  2. Do all questions. Place your answers on the exam sheets; use additional pages if necessary.
  3. The value of each part is as indicated. TOTAL Value: 100 marks
- 

**THIS EXAMINATION PAPER INCLUDES 3 PAGES AND 3 QUESTIONS. YOU ARE RESPONSIBLE FOR ENSURING THAT YOUR COPY OF THE PAPER IS COMPLETE. BRING ANY DISCREPANCY TO THE ATTENTION OF YOUR INVIGILATOR.**

---

1. [30 marks total] An electric car is designed to run off a bank of 12-V batteries (connected in parallel) with total energy storage of  $2.0 \times 10^7$  J.
  - a. If the electric motor draws 8.0 kW, what is the current delivered to the motor?
  - b. If the electric motor draws 8.0 kW, as the car moves at a steady speed of 20 m/s, how far will the car travel before it is "out of juice"?

### Solution

(a) Since  $P = VI$  
$$I = \frac{P}{V} = \frac{8.0 \times 10^3 \text{ W}}{12 \text{ V}} = 667 \text{ A}$$


(b) We find the time the car runs from 
$$P = \frac{U}{t}$$

$$t = \frac{U}{P} = \left( \frac{2.0 \times 10^7 \text{ J}}{8.0 \times 10^3 \text{ W}} \right) \left( \frac{1 \text{ W} \cdot \text{s}}{\text{J}} \right) = 2.5 \times 10^3 \text{ s}$$

So it moves a distance of

$$x = vt = (20 \text{ m/s})(2.5 \times 10^3 \text{ s}) = 50 \text{ km}$$

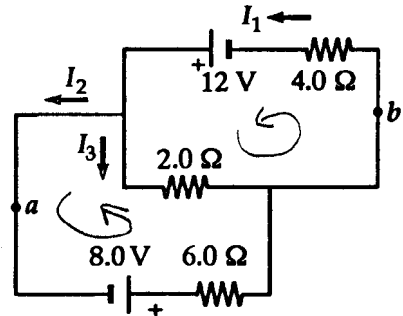2. [30 marks] For the circuit shown in the figure, calculate
- the current in the  $2.0\text{-}\Omega$  resistor and
  - the potential difference between points  $a$  and  $b$ .
- [Hint: start by picking current directions and loop directions, as shown.]



**Solution** Arbitrarily choose current directions as labeled in the figure to the right.

- (a) From the junction point rule, we have

$$I_1 = I_2 + I_3 \quad (1)$$

Traversing the top loop counterclockwise gives

$$(12\text{ V}) - (2.0\ \Omega)I_3 - (4.0\ \Omega)I_1 = 0 \quad (2)$$

Traversing the bottom loop counterclockwise,

$$8.0\text{ V} - (6.0\ \Omega)I_2 + (2.0\ \Omega) I_3 = 0 \quad (3)$$

From Equation (2),

$$I_1 = (3.0\text{ A}) - \frac{I_3}{2.0}$$

From Equation (3),

$$I_2 = \frac{(4.0\text{ A}) + I_3}{3.0}$$

Substituting these values into Equation (1), we find that  $I_3 = 0.909\text{ A}$ .

Therefore, the current in the  $2.0\text{-}\Omega$  resistor is  $0.91\text{ A}$   $\diamond$

- (b)  $V_a - (0.909\text{ A})(2.0\ \Omega) = V_b$ ,

Therefore,  $V_a - V_b = 1.8\text{ V}$ , with  $V_a > V_b$   $\diamond$

3. [40 marks] Consider a series RLC circuit having the following circuit parameters:  $R = 200 \Omega$ ,  $L = 663 \text{ mH}$ , and  $C = 26.5 \mu\text{F}$ . The applied voltage has an amplitude of  $50.0 \text{ V}$  and a frequency of  $60.0 \text{ Hz}$ . Find the following amplitudes:
- The current  $i$ , including its phase constant  $\phi$  relative to the applied voltage.
  - The voltage  $V_R$  across the resistor and its phase relative to the current.
  - The voltage  $V_C$  across the capacitor and its phase relative to the current.
  - The voltage  $V_L$  across the inductor and its phase relative to the current.

**Solution** We identify that

$$R = 200 \Omega, L = 663 \text{ mH}, C = 26.5 \mu\text{F}, \omega = 377 \text{ rad/s}, \text{ and } V_{\max} = 50 \text{ V}$$

So  $\omega L = 250 \Omega$ , and  $\left(\frac{1}{\omega C}\right) = 100 \Omega$

The impedance is

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{(200 \Omega)^2 + (250 \Omega - 100 \Omega)^2} = 250 \Omega$$

$$(a) \quad I = \frac{V}{Z} = \frac{50 \text{ V}}{250 \Omega} = 0.200 \text{ A} \quad \diamond$$

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = 36.8^\circ \quad \diamond \quad \text{with } V \text{ leading } I$$

$$(b) \quad V_R = IR = 40.0 \text{ V} \text{ at } \phi = 0^\circ \quad \diamond$$

$$(c) \quad V_C = IX_C = (0.200 \text{ A})(100 \Omega) = 20.0 \text{ V} \text{ at } \phi = -90.0^\circ \quad \diamond$$

$$(d) \quad V_L = IX_L = (0.200 \text{ A})(250 \Omega) = 50.0 \text{ V} \text{ at } \phi = 90.0^\circ \quad \diamond$$