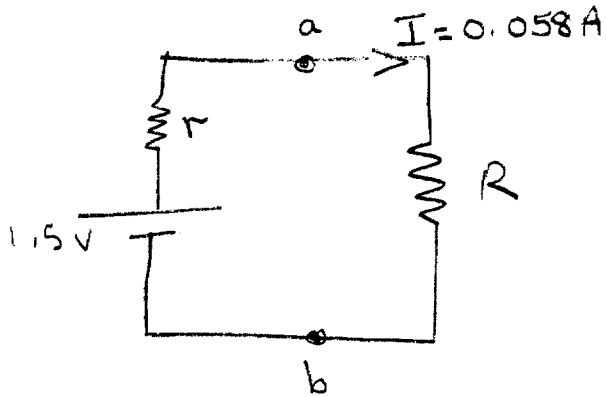


1. [Serway Chapter 28 Problem 6, pg 821]

A typical fresh AA dry cell has an emf of 1.50 V and an internal resistance of 0.311 Ω .

(a) Find the terminal voltage of the battery when it supplies 58 mA to a circuit. (b) What is the resistance R of the external circuit?



(a) Terminal voltage (ie across a b):

$$V_{ab} = 1.5 - I r$$

$$= 1.5 - 0.311 - 0.058$$

$$= \underline{\underline{1.482 \text{ V}}}$$

$$(b) R = \frac{V_{ab}}{I} = \frac{1.482 \text{ V}}{0.058 \text{ A}} = \underline{\underline{25.55 \Omega}}$$

2. [Serway Chapter 28 Problem 12, pg 821]

(a) You need a 45-Ω resistor, but the stockroom has only 20-Ω and 50-Ω resistors. How can the desired resistance be achieved under the circumstances?

(b) What can you do if you need a 35-Ω resistor?

(a) Recall that resistors in series add, i.e.:

$$R_T = R_1 + R_2 + \dots$$

While resistors in parallel follow:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$


Note that if $R_1 = R_2$ we get

$$\frac{1}{R_T} = \frac{2}{R_1} \Rightarrow R_T = \frac{1}{2} R_1$$


i.e. two like resistances in parallel cuts the resistance in half.

Now, $\frac{1}{2}$ of 50 is 25, which is just what we need.

∴ wire up as follows:

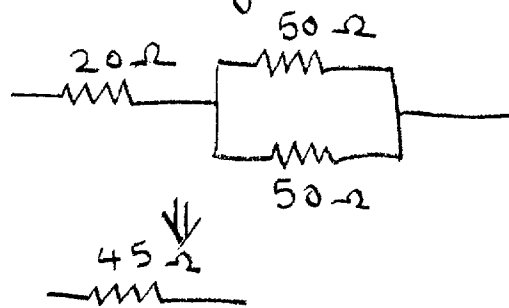


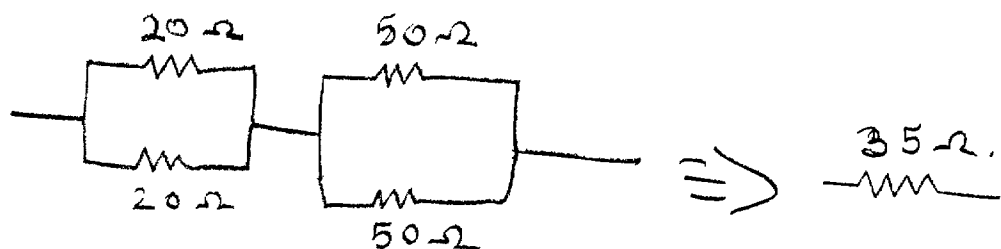(b) To get 35 Ω, put 2-20's in parallel to give 10 Ω and 2-50's in parallel to give 25 Ω. Thus:




3. [Serway Chapter 28 Problem 22, pg 822]
 The resistance between points a and b in the figure drops to $\frac{1}{2}$ its original value when S is closed. Determine the value of R.



When the switch is open the circuit is

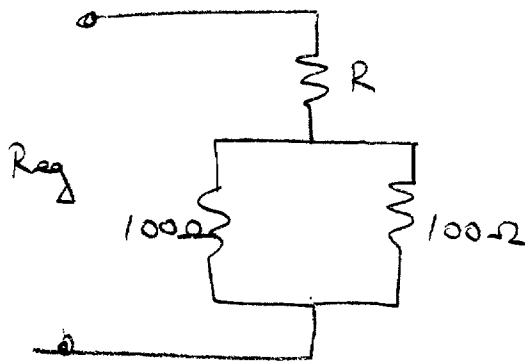

$$\Rightarrow R_{eq} = R + 50 \Omega$$

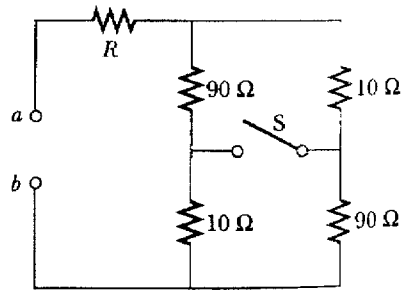

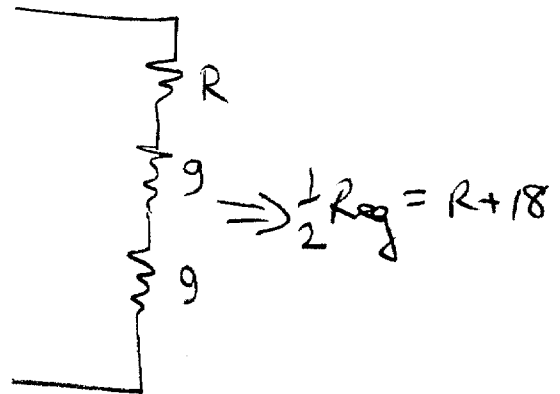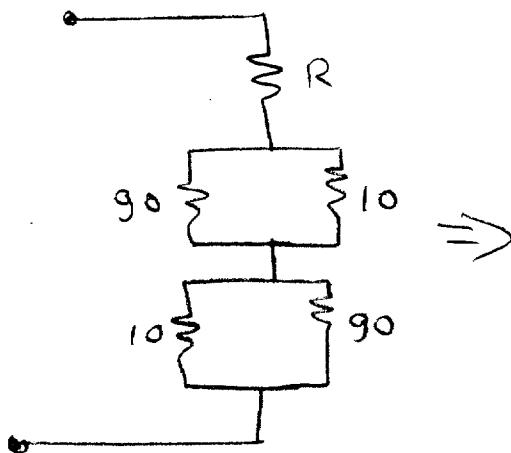When the switch is closed, the circuit is



$$\Rightarrow \frac{1}{2} R_{eq} = R + 18$$

ie $R_{eq} = R + 50$

$$\frac{1}{2} R_{eq} = R + 18 \Rightarrow R_{eq} = 2R + 36$$

Subtracting the two equations:

$$0 = -R + 14 \Rightarrow \underline{\underline{R = 14 \Omega}}$$

4. [Serway Chapter 28 Problem 29, pg 823]
 A dead battery is charged by connecting it to the live battery of another car as shown.
 Determine the current in the starter and the dead battery.

Loop 1

$$12 - 0.01 I_1 + 1.00 I_3 - 10 = 0 \quad \leftarrow \textcircled{1}$$

Loop 2

$$10 - 1.00 I_3 - 0.06 I_2 = 0 \quad \leftarrow \textcircled{2}$$

Junction

$$I_1 + I_3 = I_2 \quad \Rightarrow \quad I_1 = I_2 - I_3 \quad \textcircled{3}$$

Substituting $\textcircled{3}$ into $\textcircled{1}$:

$$12 - 0.01(I_2 - I_3) + I_3 - 10 = 0$$

ie $2 - 0.01 I_2 + 1.01 I_3 = 0 \quad \textcircled{4}$

Now: $\textcircled{2} - 6 \times \textcircled{4}$ gives:

$$10 - 0.06 I_2 - I_3 = 0$$

$$-12 + 0.06 I_2 + 6.06 I_3 = 0$$


$$-2 - 7.06 I_3 = 0$$

$$\therefore I_3 = -\frac{2.00}{7.06} = -0.283 \text{ A} = \text{current in battery}$$

ie opposite the direction shown.


$$\therefore \text{from } \textcircled{2}: I_2 = \frac{10 - I_3}{0.06} = \frac{10.283}{0.06} = \underline{171.39 \text{ A}}$$

in starter in direction shown

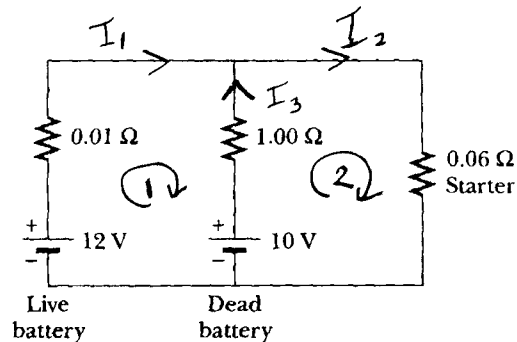


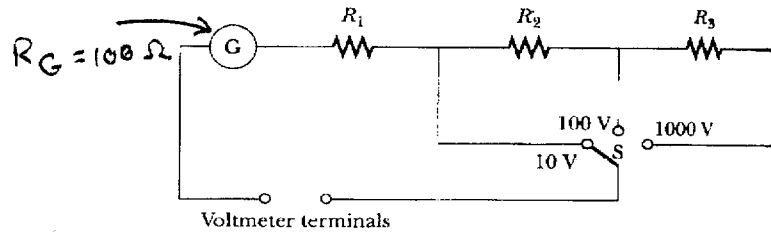5. [Serway Chapter 28 Problem 54, pg 826]

For each voltage setting, a galvanometer having an internal resistance of 100Ω deflects full scale when the current is 1.0 mA . For the multiscale voltmeter in the figure, what are the values of R_1 , R_2 and R_3 ?



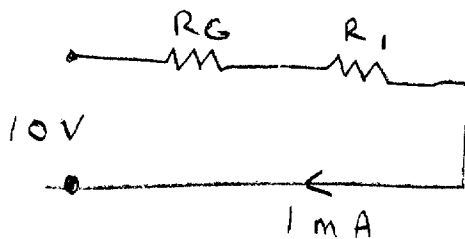
When the switch is in the 10 V position, get 1 mA full scale, i.e. 1 mA at 10 Volts .



$$\therefore 10 = (R_G + R_1) (0.001) = (100 + R_1) (0.001)$$

$$\therefore R_1 = \frac{10 - 0.1}{0.001} = \underline{\underline{9.9 \text{ k}\Omega}}$$

When S is in the 100 V position:

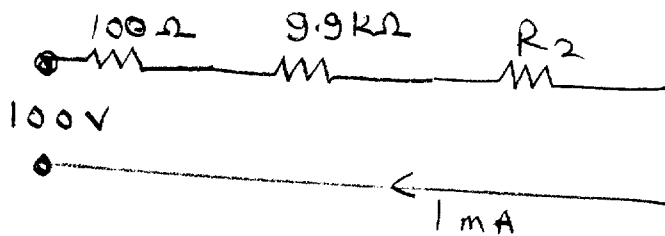

$$\begin{aligned} \therefore 100 \text{ V} &= (100 + 9,900 + R_2) (0.001) \\ &= (10,000 + R_2) (0.001) \end{aligned}$$

$$\therefore R_2 = \frac{100 - 10}{.001} = \underline{\underline{90 \text{ k}\Omega}}$$


✦ Finally, For the 1000 V case:

$$1000 = (100 + 9,900 + 90,000 + R_3) (.001)$$

$$\begin{aligned} \therefore R_3 &= \frac{(1000 - 100,000 \times .001)}{(.001)} \\ &= \underline{\underline{900 \text{ k}\Omega}} \end{aligned}$$

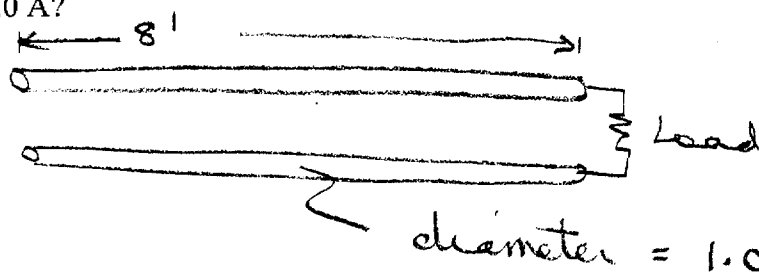6. [Serway Chapter 28 Problem 67, pg 827]

An 8-foot extension cord has two 18-gauge copper wires, each having a diameter of 1.024 mm. How much power does this cord dissipate when carrying a current of (a) 1.0 A and (b) 10.0 A?



$$\rho = 1.7 \times 10^{-8} \Omega \cdot \text{m}$$

from Serway
table 27.1

$$\text{For one wire, } R = \frac{\rho L}{A} = \frac{1.7 \times 10^{-8} \Omega \cdot \text{m} \times 16' \times 0.3048 \text{ m/ft}}{\pi \left(\frac{1.024 \times 10^{-3}}{2} \right)^2} = 0.101 \Omega$$

$$(a) \quad I = 1.0 \text{ A} \quad \therefore P = I^2 R = 1^2 (0.101) = \underline{\underline{0.101 \text{ W}}}$$

$$(b) \quad I = 10.0 \text{ A} \quad \therefore P = I^2 R = (10)^2 \times (0.101) = \underline{\underline{10.1 \text{ W}}}$$

(At 10 A, you'd feel the heat generated - so it is not a good idea to push this much current through an extension cord of this type. Use one with a heavier gauge wire.)